

תשובות סופיות לבחינת מה"ט בתורת החשמל – קיץ 2024 מועד ב'

שאלה 1

א. $U_{I_S} = 0.571(V)$

ב. $P_{I_S} = 1.714(mW)$


$P_{E_1} = 61.714(mW)$

$P_{E_2} = 3.047(mW)$


ג. $\sum P = \sum P_{נצרך} = \sum P_{מושקע}$
 $64.761mW = 64.761mW$

שאלה 2

א.

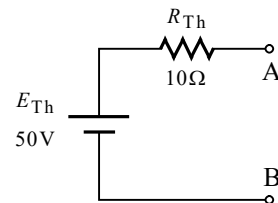

ב.

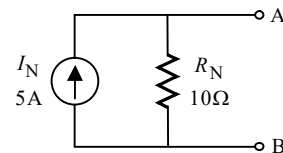

ג. $R_L = R_{Th} = 10(\Omega)$

$P_{R_L} = 62.5(W)$

ד. $R_A = 2.5(\Omega)$

ה. $I = 3.333(A)$ טעינה (צרכן)

שאלה 3

א. $\bar{U}_{Z_3} = 30.388\angle 41.15^\circ(V)$

ב. $\bar{U}_{I_S} = 73.864\angle 10.93^\circ(V)$

ג. $P_{I_S} = 698.148(W)$

$Q_{I_S} = 241.219(VAR)$

$S_{I_S} = 738.645(VA)$

שאלה 4

א. $\bar{I}_R = 23\angle 0^\circ(A)$

$\bar{I}_S = 23\angle -120^\circ(A)$

$\bar{I}_T = 23\angle -240^\circ(A)$

$\bar{U}_{RS} = 398.371\angle 30^\circ(V)$

$\bar{U}_{ST} = 398.371\angle -90^\circ(V)$


$\bar{U}_{TR} = 398.371\angle 150^\circ(V)$

ב. $P_T = 15870(W)$

$Q_T = 0(VAR)$

$S_T = 15870(VA)$

ג.

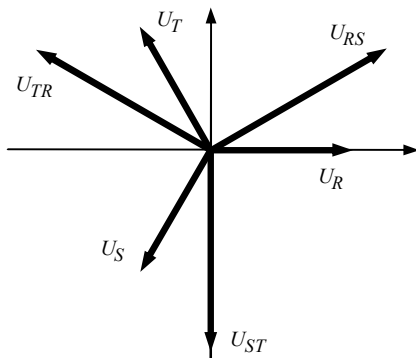

שאלה 5

א. $\bar{I}_{Z_2} = 2\angle 0^\circ(A)$

$\bar{U}_{Z_2} = 200\angle 53.13^\circ(V)$


ב. $\bar{E} = 313.190\angle 94.32^\circ(V)$

ג. $P_T = 1629.938(W)$

$Q_T = 171.476(VAR)$

$S_T = 1638.933(VA)$

ד. $PF = 0.994$

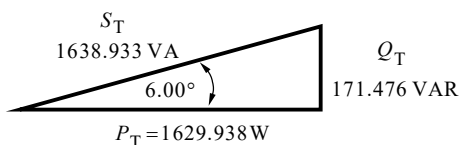

שאלה 6

$$Q_{C_1} = 16(\mu\text{C})$$

$$Q_{C_2} = 5.333(\mu\text{C})$$

$$Q_{C_3} = 5.333(\mu\text{C})$$

$$Q_{C_4} = 5.333(\mu\text{C})$$

$$Q_{C_5} = 16(\mu\text{C})$$

$$W_{L_1} = 0.036(\text{J}) = 36(\text{mJ}) \quad \text{א.}$$

$$W_C = 0.303(\text{J}) = 303.75(\text{mJ}) \quad \text{ב.}$$

$$W_T = 1.8(\text{kWh}) \quad \text{ג.}$$

$$W_{L_1} = W_{L_2} = 0.144(\text{J}) = 144(\text{mJ}) \quad \text{ד.}$$

$$W_C = 0.135(\text{J}) = 135(\text{mJ})$$

$$U_{C_x} = E = 60(\text{V}) \quad \text{ה.}$$

שאלה 9

א. מדובר בגל משולש סימטרי.

$$f = 200000(\text{Hz}) = 200(\text{kHz})$$

$$U_{\text{av}} = 0(\text{V}) \quad \text{ב.}$$

$$I_{\text{av}} = 0(\text{A})$$

$$U_{\text{rms}} = 115.47(\text{V}) \quad \text{ג.}$$

$$I_{\text{rms}} = 0.23(\text{A})$$

$$P_{\text{av}} = 26.666(\text{W}) \quad \text{ד.}$$

$$P_{\text{av}} = 31.666(\text{W}) \quad \text{ה.}$$

שאלה 7

$$\mu_{r_A} = 3183.098 \quad \text{א.}$$

$$\mu_{r_B} = 1492.077$$

$$\mu_{r_C} = 716.197$$

$$R_{m_A} = 131.25 \times 10^3 \left(\frac{1}{\text{H}} \right) \quad \text{ב.}$$

$$R_{m_B} = 280 \times 10^3 \left(\frac{1}{\text{H}} \right)$$

$$R_{m_C} = 611.111 \times 10^3 \left(\frac{1}{\text{H}} \right)$$

$$R_{m_T} = 1.022 \times 10^6 \left(\frac{1}{\text{H}} \right)$$

$$I = 0.321(\text{A}) = 321.25(\text{mA}) \quad \text{ג.}$$

שאלה 10

$$U_{C_1} = 7.5(\text{V}) \quad \text{א.}$$

$$U_{C_2} = 37.5(\text{V})$$

$$W_{C_1} = 0.562(\text{mJ}) \quad \text{ב.}$$

$$W_{C_2} = 21.093(\text{mJ})$$

$$W_L = 16(\text{nJ})$$

$$P_{I_S} = 0.15(\text{W}) \quad \text{ג.}$$

$$U_{C_1} = 60(\text{V}) \quad \text{ד.}$$

$$W_{C_1} = 36(\text{mJ})$$

$$U_{C_2} = 0(\text{V})$$

$$W_{C_2} = 0(\text{J})$$

שאלה 8

$$W_L = 0.12(\text{J}) \quad \text{א.}$$

$$U_{AB} = 8(\text{V})$$

$$U_{I_S} = 80(\text{V}) \quad \text{ב.}$$

$$P_{I_S} = 400(\text{W})$$

$$U_{C_1} = 4(\text{V}) \quad \text{ג.}$$

$$U_{C_2} = 2.666(\text{V})$$

$$U_{C_3} = 2.666(\text{V})$$

$$U_{C_4} = 2.666(\text{V})$$

$$U_{C_5} = 1.333(\text{V})$$